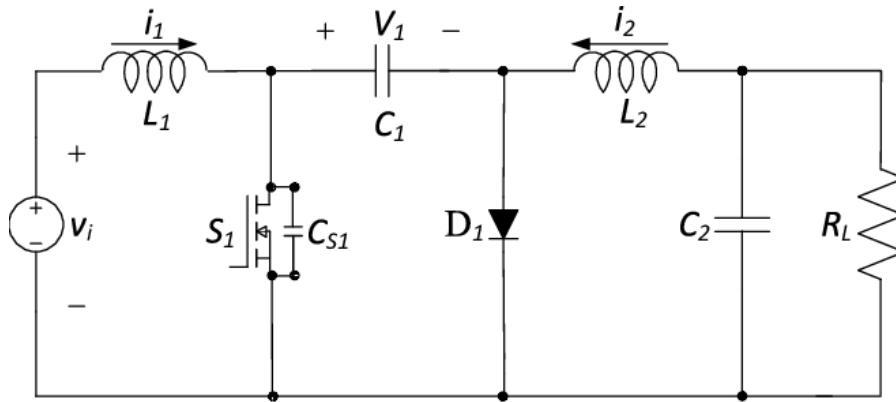


## Design of Ćuk converter



### Design parameter:

Input Voltage ( $V_{in}$ ) = 25V

Output Voltage required ( $V_o$ ) = -30V

Output Resistor ( $R$ ) = 15 Ohm

Switching Frequency = 50kHz

Output Power ( $P_o$ ) = 60W

### Step 1: Determine the Duty Ratio

$$D = \frac{V_o}{V_{in} + V_o} = 0.545$$

### Step 2: Determine the average inductor current and change in inductor currents

$$I_{l2} = \frac{P_o}{-V_o} = 2 \text{ A}$$

$$I_{l1} = \frac{P_{in}}{V_{in}} = \frac{(V_{in})^2 R}{V_{in}} = 1.66 \text{ A}$$

The change in inductor current is given by (assuming 20% changes in ripple current)

$$\Delta I_{l1} = 0.2 \times 1.66 = 0.332 \text{ A}$$

$$\Delta I_{l2} = 0.2 \times 2 = 0.4 \text{ A}$$

### Step 3: Determine Inductor Size

$$\Delta i_l = \frac{VinD}{Lf}$$

From the above equation we can calculate inductance values as:

$$L_1 = \frac{VinD}{\Delta i_{l1}f} = 820\mu H$$

$$L_2 = \frac{VinD}{\Delta i_{l2}f} = 681\mu H$$

### Step 4: Determine Capacitor size

(Assuming 1% ripple)

$$C_2 = \frac{1 - D}{8L_2 \left( \frac{\Delta V_o}{V_o} \right) f^2} = 3.33\mu F$$

Average voltage across  $C_1$  is  $25 - (-30) = 55V$

Maximum change in  $V_{C_1} = 55 \times 0.05V = 2.75V$  (Assuming ripple for  $C_1$  as 5%)

$$C_1 = \frac{VinD}{Rf\Delta V_{c1}} = 7.92\mu F$$

Choose  $C_1 = 8\mu F$  and  $C_2$  as  $3.5\mu F$